

Roll No. 6160130030

Total No. of Questions : 9]  
(1049)

[Total No. of Printed Pages : 7

**B.C.A. (CBCS) RUSA IInd Semester  
Examination**

**4387**

**DIGITAL ELECTRONICS**

Paper : BCA-0203

**Time : 3 Hours]**

**[Maximum Marks : 70**

*Note :-* Attempt *five* questions in all, selecting one question each from Unit-I to Unit-IV. Part-A (Q. No. 1) is compulsory.

**Part-A**

**(Compulsory Question)**

1. (A) Attempt all parts. Select the correct option for MCQ's.

(i) The output of an AND gate with 3-inputs A, B and C is HIGH when :

(a)  $A = 1, B = 1, C = 0$

**CH-713**

( 1 )

Turn Over

(b)  $A = 0, B = 0, C = 0$

(c)  $A = 1, B = 0, C = 0$

(d)  $A = 1, B = 1, C = 1$

8.

(ii) When used with an IC, what does the term 'QUAD' indicate ?

(a) 2 circuits

(b) 4 circuits

(c) 8 circuits

(d) 6 circuits

9

(iii) The format used to present the logic output for the various combinations of logic inputs to a gate is called a (an) :

(a) Boolean Constant

(b) Boolean Variable

(c) Truth Table

(d) Input Logic Function

(viii) On the Master-Slave flip-flop, when it is master enabled ?

- (a) When the gate is HIGH
- (b) When the gate is LOW
- (c) Both of these
- (d) None of these

(ix) Under normal conditions a diode conducts current when it is :

- (a) Reverse biased
- (b) Forward biased
- (c) Saturated
- (d) Avalanched

(x) An *n*-type semiconductor material :

- (a) is intrinsic
- (b) has trivalent impurity atoms added
- (c) has pentavalent impurity atoms added
- (d) requires no doping

$$1 \times 10 = 10$$

**H-713**

( 4 )

(iv) Which of the following expressions is in the sum-of-products (SOP) form ?

(a)  $(A + B)(C + D)$

(b)  $(A) B (CD)$

(c)  $AB + CD$

(d)  $AB (CD)$

(v) The commutative law of Boolean addition states that  $A + B = A \times B$ . (True/False)

(vi) The Boolean expression  $C + CD$  is equal to .....

(vii) When transistors are used in digital circuits they usually operate in the :

(a) active region

(b) breakdown region

(c) saturation and cutoff regions

(d) linear region

- (b) Give the circuit diagram of XOR gate. Also give its truth table. 4,6
5. (a) How can you connect NAND gates to get an OR gate ?
- (b) What are the two basic rules used to draw equivalent gates ? 6,4

### Part-D

### (Unit-III)

6. (a) Simplify the following function in sum-of-product SOP form using four variable Karnaugh's map :
- $$F(A, B, C, D) = \sum m(0, 1, 2, 3, 4, 5, 7, 11, 15)$$
- (b) What are redundant groups in K-map ? 8,2
7. (a) Explain how basic gates can be realized using NAND gates. Also give the diagram.
- (b) What do you mean by Combinational Circuit ? 6,4



(B) Answer the following in 25 to 50 words :

- (i) State the associative property of Boolean Algebra.
- (ii) What is meant by Karnaugh map method ?
- (iii) State advantages and disadvantages of TTL.
- (iv) What is a Decoder ?
- (v) Define Minterm and Maxterm. 4×5=20

### Part-B

#### (Unit-I)

- 2. (a) Discuss the working of  $p-n$  junction diode.
- (b) Explain energy bands in solids. 5,5
- 3. (a) Discuss Saturated and Non-saturated Logic.
- (b) Which is faster ECL or TTL ? Explain. 5,5

### Part-C

#### (Unit-II)

- 4. (a) Simplify the expressions using Boolean Algebra :
  - (i)  $A\bar{B}C + ABC$
  - (ii)  $(\bar{A} + B + C)(A + B + \bar{C})$

**Part-II****(Unit-IV)**

8. (a) What is a Multiplexer ? Explain difference between MUX and DEMUX.
- (b) What do you mean by Shift-Registers ? Discuss. 5,5
9. (a) Explain the working and circuit of a Half-Adder.
- (b) Give the design of  $3 \times 8$  decoder. 6,4