

Roll No. ....

Total No. of Questions : 9] [Total No. of Printed Pages : 7  
(2043)

**B.C.A. (CBCS) RUSA IInd Semester  
Examination**

**4207**

**DIGITAL ELECTRONICS**

Paper : BCA-0203

**Time : 3 Hours]**

**[Maximum Marks : 70**

- Note :-** (i) Question No. 1 (Part-A) is compulsory. Attempt *four* questions choosing *one* question each from Parts-B, C, D and E.
- (ii) Figures at the right indicate marks.

**Part-A**

**(Compulsory Question)**

- I. (A) Select the correct alternative for MCQs.
- (i) Under normal conditions a diode conducts current when it is .....
- (a) reverse biased

**CA-743**

( 1 )

Turn Over

- (b) forward biased
  - (c) avalanched
  - (d) saturated
- (ii) In the toggle mode, a J-K flip-flop has :
- (a)  $J = 0, K = 1$
  - (b)  $J = 1, K = 1$
  - (c)  $J = 0, K = 0$
  - (d)  $J = 1, K = 0$
- (iii) De Morgan's law states that :
- (a)  $(A + B)' = A' * B$
  - (b)  $(AB)' = A' + B'$
  - (c)  $(AB)' = A' + B$
  - (d)  $(AB)' = A + B$
- (iv) A K-map is an abstract form of which diagram organized as a square matrix :
- (a) Block diagram
  - (b) Cycle diagram
  - (c) Square diagram
  - (d) Venn diagram

- (v) TTL is a class of digital circuits built from :
- (a) Resistors only
  - (b) JEFT only
  - (c) BJT only
  - (d) Both (a) and (c)
- (vi) The basic storage element in a digital system is .....
- (a) flip-flop
  - (b) counter
  - (c) multiplexer
  - (d) encoder
- (vii) What will be the output from a D flip-flop if the clock is low and  $D = 0$  ?
- (a) 0
  - (b) 1
  - (c) No change
  - (d) Toggle between 0 and 1

(viii) Which of these sets of logic gates are known as universal gates ?

- (a) XOR, NAND, OR
- (b) OR, NOT, XOR
- (c) NOR, NAND, XNOR
- (d) NOR, NAND

(ix) A combinational circuit does not have

.....

(x) Number of inputs for a full adder is

.....

1×10=10

(B) Answer the following in 25 to 50 words :

- (i) Distinguish between De-multiplexer and decoder.
- (ii) Write a short note on don't care condition.
- (iii) Give the applications and advantages of CMOS.
- (iv) Explain BCD adder.
- (v) Explain energy bands in solids. 4×5=20

CA-743

( 4 )

### Part-B

(Unit-I)

10 each

- 2. Discuss in detail the forward and reverse bias in *p-n* junction diode with suitable diagram.
- 3. What are digital logic families ? Compare all logic families and their characteristics.

### Part-C

(Unit-II)

10 each

- 4. Simplify the following expressions using Boolean algebra :

(i)  $Y = (A + B) (A + B') (A' + B')$

(ii)  $Y = (C + D)' + A'CD' + (ABC)'$

$+ ABCD' + ACD'$

- 5. Discuss NOR, NAND and XOR gates in detail with truth table and symbols.

CA-743

( 5 )

Turn Over

**Part-D**

**(Unit-III)**

10 each

6. Given :

$$F(A, B, C, D) = \Sigma(0, 2, 3, 6, 7, 12, 13, 14) \\ + d(1, 4, 11, 15)$$

where  $d$  denotes the don't care condition.

Find simplified expression :

- (i) In SOP form
  - (ii) In POS form, also realize the simplified expression using gates.
7. Define Combinational circuits. Discuss in detail the Karnaugh-map technique with suitable example.

**Part-E**

**(Unit-IV)**

10 each

8. Draw and write the truth table of J-K flip-flop. What is race around condition in J-K flip-flop ? How can it be avoided ?

**CA-743**

( 6 )

9. Describe the need of a multiplexer in a system. Draw the logic diagram of  $8 \times 1$  multiplexer and  $2 \times 4$  decoder.

**CA-743**

( 7 )