

Pihu KashyapTotal No. of Questions : 9]
(1056)

[Total No. of Printed Pages : 4

BCA (CBCS) IInd Semester Examination

7074**DIGITAL ELECTRONICS****BCA-203**

Time : 3 Hours]

[Maximum Marks : 70

The candidates shall limit their answers precisely within the answer-book (40 pages) issued to them and no supplementary/continuation sheet will be issued.

Note :- Attempt any *five* questions in all. Select *one* question each from Units I, II, III and IV. Unit V (Q. No. 9) is compulsory.

Unit-I

1. (a) Discuss the characteristics of transistor-transistor logic and emitter-coupled logic digital families. 9
- (b) Write short notes on Integrated circuits. 5
2. (a) Explain the forward and reverse biasing of p-n junction. 10
- (b) Explain valence and conduction bonds in solids. 4

H-69

(1)

Turn Over

Unit-II

3. (a) Prove the following expressions using Boolean algebra :

(i) $(A + B) \cdot (\bar{A} + C) = AC + \bar{A}B$ 7

(ii) $A + \bar{A}B + A\bar{B} = A + B$

(b) Give the logic symbol and truth tables for the following combinational gates :

(i) Exclusive OR gate

(ii) Exclusive NOR gate 7

4. (a) Explain basic Boolean Law's with suitable examples. 5

(b) Apply Demorgan's theorem to the following expressions :

(i) $\overline{(W + X)Y}$

(ii) $\overline{(A + \bar{B} + C + \bar{D})}$

(iii) $\overline{\bar{X} + \bar{Y} + \bar{Z}}$ 9

Unit-III

5. (a) Simplify the following Boolean function by using K-map and implement it using NoR gates.

$f(ABCD) = \sum m(2, 3, 4, 5, 6, 7, 11, 14, 15)$ 10

- (b) Give the sum of Product expression of AND-OR realization. 4
6. (a) Explain the minimization technique for 4-variables by giving minterms and maxterms. 7
- (b) Distinguish between algebraic method and Karnaugh method for minimisation of Boolean expressions. 7

Unit-IV

7. (a) Give the logic diagram and truth table for a Half-Adder. 8
- (b) What is an encoder ? Give the truth table for octal to binary encoder. 6
8. (a) What is a sequential circuit ? Explain its types. 6
- (b) Give the construction of Master-Slave JK flip-flop. 8

Unit-V (Compulsory Question)

9. Attempt all parts :
- (i) Define K-Map.
- (ii)is a universal gate.
- (iii) Differentiate between intrinsic and extrinsic semiconductors.

H-69

(3)

Turn Over

- (iv) Explain race around conditions in flip-flops.
- (v) Give the truth table for NAND gate.
- (vi) Write the Boolean expression for a 2-input NOR gate.
- (vii) Simplify $Y = \bar{A}Q + AQ$

2×7=14