

Roll No. 6160130030.

Total No. of Questions : 9]
(1048)

[Total No. of Printed Pages : 3

**B.C.A. (CBCS) RUSA IInd Semester
Examination****4029****DIGITAL ELECTRONICS**

Paper : BCA-0203

Time : 3 Hours]**[Maximum Marks : 70**

Note :- Attempt five questions in all. Select one question from each Unit-I, II, III and IV. Question No. 9 (Unit-V) is compulsory.

Unit-I

1. (a) Explain Band theory in solids.
- (b) Discuss forward and reverse biasing of a $p-n$ junction. 7,7
2. (a) Explain the characteristics of TTL, CMOS and ECL logic families.
- (b) Explain the working of Bipolar Junction Transistor. 8,6

C-661

(1)

Turn Over

Unit-II

3. (a) Explain basic logic gates and also give their truth tables.

(b) State and explain deMorgan's theorem. 8,6

4. (a) Simplify the following using Boolean Algebra :

(i) $\overline{AB} + \overline{AC} + \overline{ABC}$

(ii) $A + \overline{AB} + \overline{AB}$

(iii) $(A + B)(\overline{A} + C)$

(b) What are universal gates ? Show that NAND is a universal gate. 6,8

Unit-III

5. (a) Using four variable map, find the minimal SOP expression for the Boolean function :

$$f(w, x, y, z) = \sum m(2, 5, 7, 9, 10, 11, 13, 15)$$

(b) What is k -map ? What is the significance of pairs, quads and octets in a k -map ? 10,4

6. (a) Discuss the minimization technique for 4-variables by giving minterms and maxterms.

(b) Discuss Venn diagram by giving a suitable example. 8,6

Unit-IV

7. (a) Explain the working and logic diagram of a full adder with three inputs. 8,6
- (b) Design a decimal to BCD encoder circuit.
8. (a) What is a flip-flop ? Draw the circuit diagram of JK-flip-flop using NAND gate.
- (b) What is a multiplexer ? Give the logic diagram of 4×1 multiplexer. 7,7

Unit-V**(Compulsory Question)**

9. Attempt all parts.

- (a) What is breakdown voltage ?
- (b) and are universal gates.
- (c) Give the Boolean expression for 2-input NOR gate.
- (d) What is a decoder ?
- (e) What is race-around condition in flip-flops ?
- (f) What do you mean by product of sum (POS) ?
- (g) What is CE configuration of a transistor ? $7 \times 2 = 14$

C-661

(3)

base
emitter
collector